

POT

MO

PLA

O

GIR
D. TRANSF.
OP. POJ.,
VEZAN/IZVOL

NORTON
THEVENIN

(1)

- METODA ČVOROVA
- METODA PĒTLJI
- KZN + KZS
 $\delta - \bar{c} + 1$ $\bar{c} - 1$


- NORMALIZACIJA
- POSMAK
- FAZORI

(2) MREŽE/GRAFOVI - IZ MATRICA/GRAFA \Rightarrow MREŽU
NEI OBRAUTO

(3) PRIJENOSNE KARAKTERISTIKE - NAČI $T_{SP} = \frac{U_{IZ}}{U_{UL}}$

$$|T_{SP}| : \varphi = \arg(T(j\omega))$$

$X(j\omega)$ - LOGARITANSKI

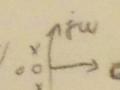- POLOVI I NULE + CRTANJE U_o 

- STABILNOST/NESTABILNOST

- CRTANJE KARAKTERISTIKE

(4) ĆETVEROPOLI - ODLEDIVANJE PARAMETARA - PREBAUVANJE IZ JEDNE U DRUGU

- T / Π SPOJ

- REAKCIJNOST
- SMOĆIĆNOST

(- SPAJANJE ĆETVEROPOLA)

(3) PRIJENOSNE KARAKTERISTIKE

$$= \text{NAČI } T_{\text{SF}} = \frac{U_{\text{SF}}}{U_{\text{NL}}}$$

$$= |T(\omega)| \text{ i } \varphi = \arg(T(j\omega))$$

$\alpha(j\omega)$ - LOGARITANSKI

$$= \text{POKAZ I NULE} + \text{CRTANJE } U_{\text{NL}} \xrightarrow{j\omega} e^{j\varphi}$$

- STABILNOST/NESTABILNOST

- CRTANJE KARAKTERISTIKE

(4) ČETVEROPOLI - ODREĐIVANJE PARAMETARA - PREBACIVANJE IZ JEONE U DRUGU

- T I Π SPOJ

- RECIPROČNOST

(- SPAJANJE ČETVEROPOLA)

- SIMETRIČNOST

(5) FILTRI - PREPOZNAVANJE FILTRA

- ODREĐIVANJE ω , Q i K

- CRTANJE KARAKTERISTIKE

(6) LINIJE



$$U(t) \rightarrow U(x, t)$$

$$I(t) \rightarrow I(x, t)$$

OPĆI POKLONI

OHMOV ZAKON

$$I = \frac{U}{Z}$$

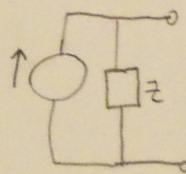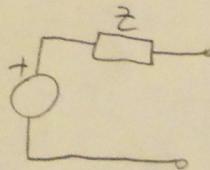

$$U \longrightarrow I = \frac{U}{Z}$$

$$U = I \cdot Z \longleftarrow I$$

$$I = \frac{\varphi_A - \varphi_B}{R}$$

ELEMENTI

$$\text{---} \square \text{---} R \quad \text{---} \circ \text{---} R$$

$$\text{---} \square \text{---} \quad U(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = U_0 + \frac{1}{C} \int_0^t i(\tau) d\tau \rightarrow I(s) = \frac{U_0}{s} + \frac{1}{sC} \cdot I(s)$$

$$Z_C \quad \text{---} \circ \text{---} \boxed{\frac{1}{sC}} \quad (i = C \cdot \frac{dU}{dt})$$

$$\text{---} \square \text{---} \quad U_L(t) = L \cdot \frac{di}{dt} \quad Z_L \quad \text{---} \circ \text{---} \boxed{s \cdot L}$$

$$i(t) = \frac{1}{L} \int_{-\infty}^t u(\tau) d\tau = i(0) + \frac{1}{L} \int_0^t i(\tau) d\tau \rightarrow I(s) = \frac{i(0)}{s} + \frac{1}{sL} \cdot I(s)$$

NORMALIZACIJA

a) IMPEDANCIJE

$$R_N = \frac{R}{R_0} = r_n \quad R = R_N \cdot R_0$$


$$sL_N = \frac{sL}{R_0} \quad sL = sL_N \cdot R_0$$

$$\frac{1}{sC_N} = \frac{1}{sC \cdot R_0} \quad sC = \frac{sC_N}{R_0}$$

b) FREKVENCIJE

$$s_M = \frac{s}{\omega_0}$$

OP. AMP.

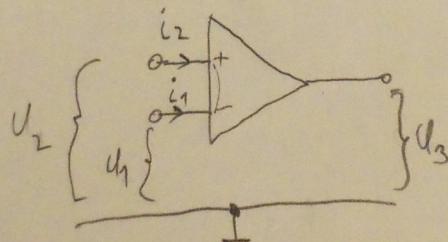

$$(u_2 - u_1) = \frac{u_3}{A} \quad \left. \right|_{A \rightarrow \infty} = 0$$

$$u_2 = u_1$$

$$i_2 = i_1 = 0$$

KIRCHHOFFOV ZAKONI

KZ - ZA STRUJE


$\bar{c}-1$

KZ - ZA NAPONE

$\bar{g}-(\bar{c}-1)$

$\bar{g}-\bar{c}+1$


KZS

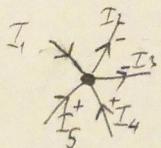

$$I_1 - I_2 - I_3 + I_4 + I_5 = 0$$


$\bar{c}-1$

KZN

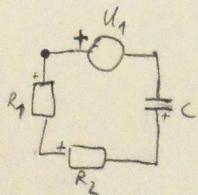

$$U_{R_1} + U_{R_2} + U_C - U_1 = 0$$

M1 - 2012/13-4)

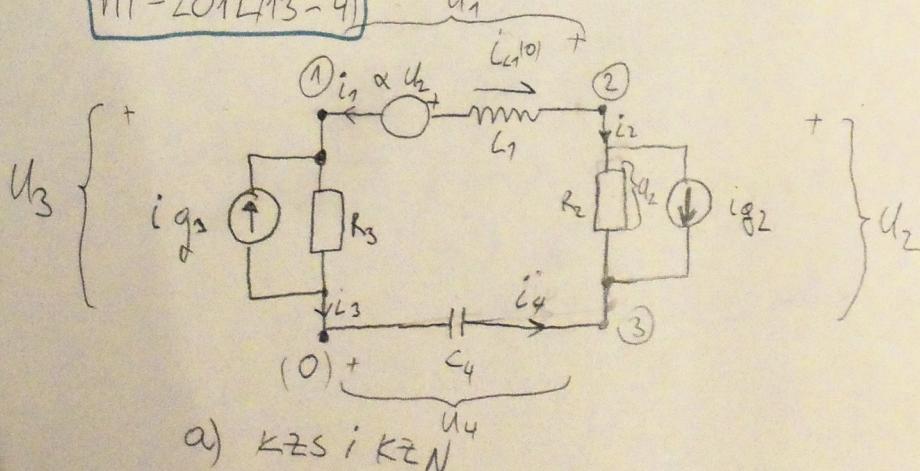

a) KZS i KZN

b) NAPONSKO-STRUJNE JEDNADŽBE ZA GRANJE

c) $U_{R_2}(s)$ i $U_{R_2}(t)$

d) $I_{R_3}(s)$ i $i_{R_3}(t)$

a)

$$\bar{c} = 4$$

$$g = 4$$

$$KZS \rightarrow \bar{c}-1 = 3 \quad \left. \begin{array}{l} \\ \end{array} \right\} 4$$

$$KZN \rightarrow g-\bar{c}+1=1 \quad \left. \begin{array}{l} \\ \end{array} \right\} 4$$

$$1) I_1 - I_3 = 0 \quad \left. \begin{array}{l} \\ \end{array} \right\}$$


$$2) I_1 + I_2 = 0 \quad \left. \begin{array}{l} \\ \end{array} \right\} KZS$$

$$3) I_2 + I_4 = 0 \quad \left. \begin{array}{l} \\ \end{array} \right\}$$

$$4) U_1 + U_3 + U_4 - U_2 = 0 \quad KZN$$


b)

1)

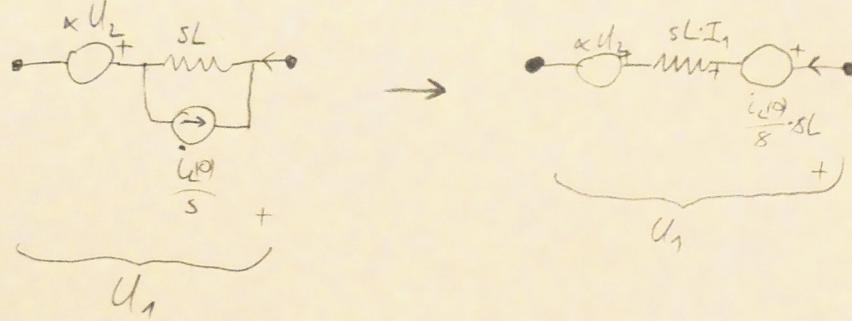


$$U_1 = i(0) \cdot L + I_1 \cdot sL + \times U_2 = i(0) \cdot L + I_1 \cdot sL + \times (I_2 - I_{g2}) \cdot R_2$$

2)

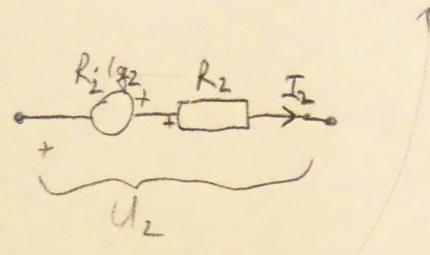

$$U_2 = I_2 \cdot R_2 - R_2 \cdot I_{g2}$$


3)

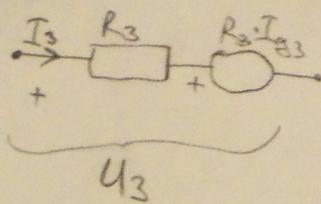

191 2012/13-4)

$$U_3 = I_3 \cdot R_3 + R_2 \cdot I_{g3}$$

4)

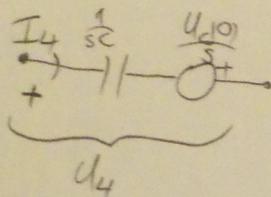

$$U_4 = I_4 \frac{1}{sC} - \frac{U_{d0}}{s}$$

c)

$$I_1 = -I_2 = I_3 = I_4$$

$$U_1 = s \cdot 1 \cdot I_1 + 1 + 2 \cdot \left(-I_1 - \frac{1}{s} \right) \cdot 1$$

$$U_1 - U_2 + U_3 + U_4 = 0$$

$$U_2 = \left(-I_1 - \frac{1}{s} \right) \cdot 1$$

$$U_3 = \left(I_1 + \frac{1}{s} \right) \cdot 2$$

$$U_4 = \frac{1}{s \cdot \frac{1}{2}} \cdot I_1 - \frac{2}{s}$$

$$sI_1 + 1 - 2I_1 - \frac{2}{s} + I_1 + \frac{1}{s} + 2I_1 + \frac{2}{s} + \frac{2}{s}I_1 - \frac{2}{s} = 0$$


$$(s - 2 + 1 + 2 + \frac{2}{s})I_1 = \frac{1}{s} - 1 \quad | \cdot s$$

$$(s^2 + s + 2)I_1 = 1 - s$$

$$I_1 = \frac{1-s}{s^2 + s + 2}$$

:

METODA NAPONA ČVOROVA

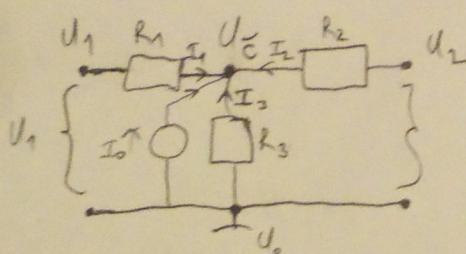


$$I = \frac{U_A - U_B}{R}$$

$$I_0 + I_1 + I_2 + I_3 = 0$$

$$I_0 + \frac{U_1 - U_C}{R_1} + \frac{U_2 - U_C}{R_2} + \frac{U_o - U_C}{R_3} = 0$$

$$U_C \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - U_1 \left(\frac{1}{R_1} \right) - U_2 \left(\frac{1}{R_2} \right) - U_o \left(\frac{1}{R_3} \right) = I_0$$

ZADATAK MI - 2012/13

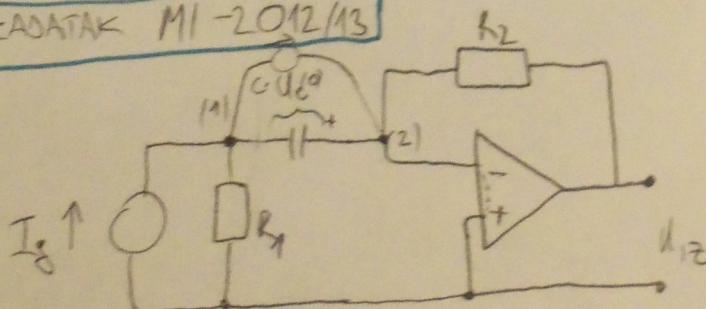


$$(1) \quad U_1 \left(\frac{1}{R_1} + SC \right) - U_2 (SC) = I_g - C \cdot U_{d0}$$

$$(2) \quad U_2 \left(SC + \frac{1}{R_2} \right) - U_1 (SC) - U_{1z} \left(\frac{1}{R_2} \right) = C \cdot U_{d0}$$

$$\therefore U_{1z} = 0$$


METODA KONTURNIH PELJU

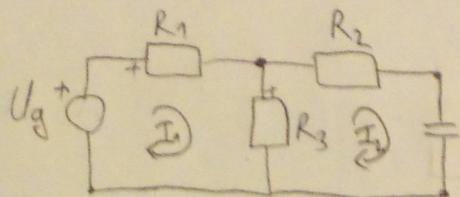

$$(1) -U_g + I_1 \cdot R_1 + (I_1 - I_2) \cdot R_3 = 0$$

$$(12) I_2 \cdot R_2 + I_2 \frac{1}{SC} - (I_1 - I_2) \cdot R_3 = 0$$

THEVENIN

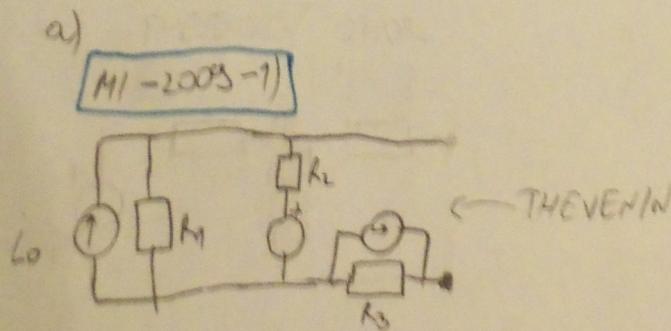


THEVENINOV OTPOR = U_{GAB}/I_{GAB} NEZAVISNE ISVREKE


I IZMENJAVAJUĆI EKVIVALENTNI OTPOR

THEVENIN NAPON = NA STELLI KADA IZMENJAVAMU OTPOR PRAZAN
PROSTOR

(MI 2005-1)

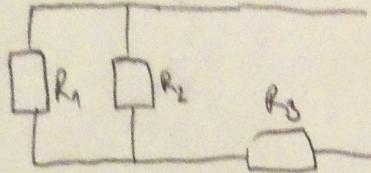


$$R_T = R_3 + R_1 \parallel R_2$$

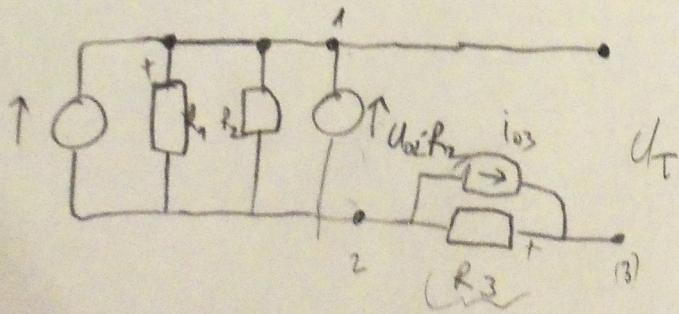

$$U_T = (i_0 + R_2 U_{02}) \cdot \left(\frac{R_1 \cdot R_2}{R_1 + R_2} \right) - I_{03} \cdot R_3$$

MI 2012/2013 -2)

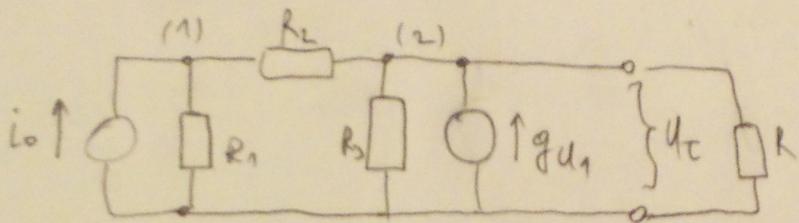

$$i_o = 2 \text{ A}$$

$$R_1 = 1 \Omega$$

$$R_2 = \frac{1}{2} \Omega$$

$$R_3 = \frac{1}{3} \Omega$$

a) U_T

$$(1) \quad U_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - U_2 \left(\frac{1}{R_2} \right) = i_o$$

$$(2) \quad U_2 \left(\frac{1}{R_2} + \frac{1}{R_3} \right) - U_1 \left(\frac{1}{R_2} \right) = g \cdot U_1$$


$$U_2 (2+3) = (g+2) U_1 \quad U_2 = \frac{g+2}{5} U_1 \quad U_1 = \frac{5}{g+2} \cdot U_2$$

$$U_1 (1+2) - U_2 (2) = 2$$

$$\frac{15}{g+2} U_2 - 2 U_2 = 2 \quad U_2 \left(\frac{15-2g-4}{g+2} \right) = 2$$

$$U_2 = \frac{2g+4}{11-2g} = U_T$$

b)

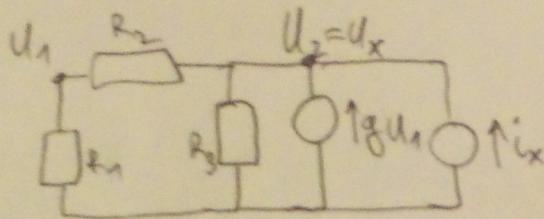

$$(1) \quad U_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - U_2 \left(\frac{1}{R_2} \right) = 0$$

$$(2) \quad U_2 \left(\frac{1}{R_2} + \frac{1}{R_3} \right) - U_1 \left(\frac{1}{R_2} \right) = g U_1 + i_x$$



$$3 \cdot U_1 = 2 U_2 \quad U_1 = \frac{2}{3} U_2$$

$$U_2 \cdot 5 - U_1 (2 + g) = i_x$$

$$U_2 \cdot 5 - \frac{2}{3} (2 + g) \cdot U_2 = i_x$$


$$U_2 \left(\frac{11 - 2g}{3} \right) = i_x \quad \frac{U_2}{i_x} = R_T = \frac{3}{11 - 2g}$$

M1 2012/2013 (5)

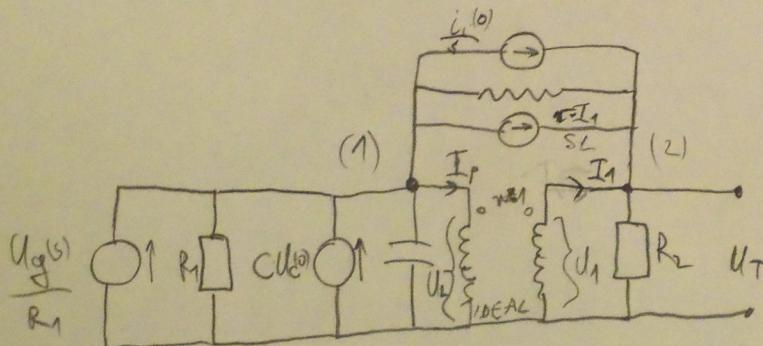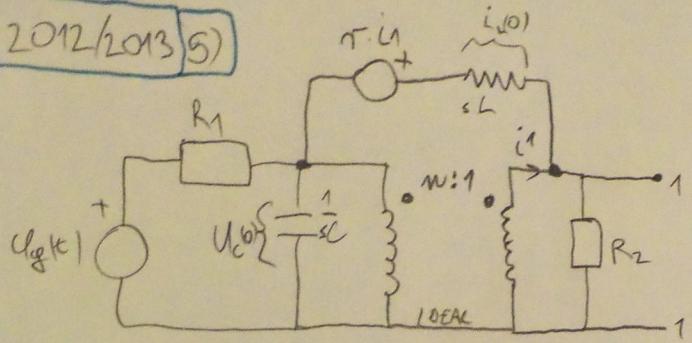

$$(1) \quad U_1 \left(sC + \frac{1}{R_1} + \frac{1}{sL} \right) - U_2 \left(\frac{1}{sL} \right) = \frac{U_g(0)}{R_1} + C U_c(0) + \frac{sI_s}{sL} - I_p$$
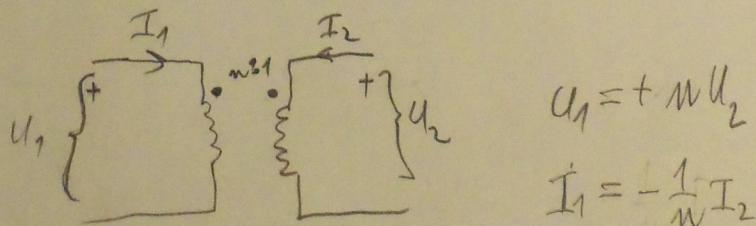
$$(2) \quad U_2 \left(\frac{1}{sL} + \frac{1}{R_2} \right) - U_1 \left(\frac{1}{sL} \right) = \frac{-sI_s}{sL} + \frac{i_1(0)}{s} + I_s$$



$$(3) \quad U_1 = n \cdot U_2$$

$$(4) \quad I_p = \frac{1}{n} I_s$$